

Synchronous FIFO Demonstration

initial				FIFO is empty
		FIFO		
	write pointer = 0		read pointer = 0	

push:	increment the write pointer		
		FIFO	
	write pointer = 1		
		data0	read pointer = 0

pop:	increment the read pointer		FIFO is empty
		FIFO	
	write pointer = 1		read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
	write pointer = 2		
		data1	read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
	write pointer = 3		
		data2	
		data1	read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
	write pointer = 4		
		data3	
		data2	
		data1	read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
	write pointer = 5		
		data4	
		data3	
		data2	
		data1	read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
	write pointer = 6		
		data5	
		data4	
		data3	
		data2	
		data1	read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
	write pointer = 7		
		data6	
		data5	
		data4	
		data3	
		data2	
		data1	read pointer = 1
		data0	

push:	increment the write pointer		
		FIFO	
		data7	
		data6	
		data5	
		data4	
		data3	
		data2	
		data1	read pointer = 1
	write pointer = 0	data0	

push:	increment the write pointer		FIFO is full
		FIFO	
		data7	
		data6	
		data5	
		data4	
		data3	
		data2	
	write pointer = 1	data1	read pointer = 1
		data0	

pop:	increment the read pointer			
		FIFO		
		data7		
		data6		
		data5		
		data4		
		data3		
		data2	read pointer = 2	
	write pointer = 1	data1		
		data0		

pop:	increment the read pointer		
		FIFO	
		data7	
		data6	
		data5	
		data4	
		data3	read pointer = 3
		data2	
	write pointer = 1	data1	
		data0	

pop:	increment the read pointer		
		FIFO	
		data7	
		data6	
		data5	
		data4	read pointer = 4
		data3	
		data2	
	write pointer = 1	data1	
		data0	

pop:	increment the read pointer		
		FIFO	
		data7	
		data6	
		data5	read pointer = 5
		data4	
		data3	
		data2	
	write pointer = 1	data1	
		data0	

pop:	increment the read pointer			
		FIFO		
		data7	read pointer = 6	
		data6		
		data5		
		data4		
		data3		
		data2		
	write pointer = 1	data1		
		data0		

pop:	increment the read pointer		
		FIFO	
		data7	read pointer = 7
		data6	
		data5	
		data4	
		data3	
		data2	
	write pointer = 1	data1	
		data0	

pop:	increment the read pointer			
		FIFO		
		data7		
		data6		
		data5		
		data4		
		data3		
		data2		
	write pointer = 1	data1		
		data0	read pointer = 0	

pop:	increment the read pointer		FIFO is empty
		FIFO	
		data7	
		data6	
		data5	
		data4	
		data3	
		data2	
	write pointer = 1	data1	read pointer = 1
		data0	

push:	increment the read pointer		
		FIFO	
		data7	
		data6	
		data5	
		data4	
		data3	
	write pointer = 2	data2	
		data1	read pointer = 1
		data0	

push AND pop:	increment both pointers		
		FIFO	
		data7	
		data6	
		data5	
		data4	
	write pointer = 3	data3	
		data2	read pointer = 2
		data1	
		data0	

Full or Empty?

	FIFO			FIFO	
	data7			data7	
	data6			data6	
	data5			data5	
	data4			data4	
	data3			data3	
	data2			data2	
write pointer = 1	data1	read pointer = 1	write pointer = 1	data1	read pointer = 1
	data0			data0	

Solution: use an extra bit to which cycle the pointer is on

write cycle = 1	FIFO	read cycle = 0	write cycle = 0	FIFO	read cycle = 0
	data7			data7	
	data6			data6	
	data5			data5	
	data4			data4	
	data3			data3	
	data2			data2	
write pointer = 1	data1	read pointer = 1	write pointer = 1	data1	read pointer = 1
	data0			data0	

FULL when write_cycle != read_cycle


EMPTY when write_cycle == read_cycle

SystemVerilog Microarchitecture Challenge

10/26/2025

The Challenge

 - Write a pipelined block that computes: $a^{**5} + 0.3*b - c$
- You may ONLY use pre-existing blocks for arithmetic operations
- Your design must achieve a throughput of 1 output per cycle when there is no backpressure
- Check your solution against a pre-existing testbench




Arithmetic Modules

- You may ONLY use pre-existing blocks for arithmetic operations

```
assign res = a + b;
```

 Not allowed

 
```
module f_add (  
    input          clk,  
    input          rst,  
    input  [FLEN - 1:0] a, b,  
    input          up_valid,  
    output [FLEN - 1:0] res,  
    output          down_valid,  
    output          busy,  
    output          error  
);
```





Instantiation of f_add

```
f_add a_plus_b (  
    .clk      ( clk      ),  
    .rst      ( rst      ),  
    .up_valid ( up_valid ),  
    .a        ( a        ),  
    .b        ( b        ),  
    .down_valid ( down_valid ),  
    .res       ( res      )  
);
```

Valid/Ready from AXI-Stream

 

  
Throughput 1 Output per Cycle and No Empty Cycle Gaps



Empty Cycle Gap (bubble) from simulation.log

***** Constraint random values back-to-back

testbench.sv	time	26200	cycle	2619	arg	a:24508.6	b:10827.4	c:758.144	
testbench.sv	time	26210	cycle	2620	arg	a:8378.34	b:22603	c:33365.4	
testbench.sv	time	26220	cycle	2621	arg	a:8516.09	b:1546.2	c:21634.7	
testbench.sv	time	26230	cycle	2622	arg	a:22622.9	b:31396.9	c:26600.9	
testbench.sv	time	26240	cycle	2623	arg	a:41411.1	b:33249	c:42445	
testbench.sv	time	26250	cycle	2624	arg	a:16645.6	b:16603.9	c:14273.6	
testbench.sv	time	26260	cycle	2625	arg	a:40716.2	b:10036.5	c:1543.27	
testbench.sv	time	26270	cycle	2626	arg	a:33541.9	b:41807	c:17358.3	
testbench.sv	time	26280	cycle	2627	arg	a:19461.9	b:16574.3	c:29250.2	
testbench.sv	time	26290	cycle	2628	arg	a:15863.7	b:3803.28	c:8498.15	
testbench.sv	time	26300	cycle	2629	arg	a:8377.72	b:22389.4	c:10776.2	
testbench.sv	time	26310	cycle	2630	arg	a:24224.8	b:35814.3	c:13220.4	
testbench.sv	time	26320	cycle	2631	arg	a:12604	b:1596.27	c:1129.98	
testbench.sv	time	26330	cycle	2632	arg	a:6988.65	b:30471.5	c:17892.7	NOT READY arg_rdy:0
testbench.sv	time	26340	cycle	2633	arg	a:6988.65	b:30471.5	c:17892.7	res:8.84292e+21

 

No Bubble

***** Constraint random values back-to-back

testbench.sv	time	26200	cycle	2619	arg	a:24508.6	b:10827.4	c:758.144	
testbench.sv	time	26210	cycle	2620	arg	a:8378.34	b:22603	c:33365.4	
testbench.sv	time	26220	cycle	2621	arg	a:8516.09	b:1546.2	c:21634.7	
testbench.sv	time	26230	cycle	2622	arg	a:22622.9	b:31396.9	c:26600.9	
testbench.sv	time	26240	cycle	2623	arg	a:41411.1	b:33249	c:42445	
testbench.sv	time	26250	cycle	2624	arg	a:16645.6	b:16603.9	c:14273.6	
testbench.sv	time	26260	cycle	2625	arg	a:40716.2	b:10036.5	c:1543.27	
testbench.sv	time	26270	cycle	2626	arg	a:33541.9	b:41807	c:17358.3	
testbench.sv	time	26280	cycle	2627	arg	a:19461.9	b:16574.3	c:29250.2	
testbench.sv	time	26290	cycle	2628	arg	a:15863.7	b:3803.28	c:8498.15	
testbench.sv	time	26300	cycle	2629	arg	a:8377.72	b:22389.4	c:10776.2	
testbench.sv	time	26310	cycle	2630	arg	a:24224.8	b:35814.3	c:13220.4	
testbench.sv	time	26320	cycle	2631	arg	a:12604	b:1596.27	c:1129.98	
testbench.sv	time	26330	cycle	2632	arg	a:6988.65	b:30471.5	c:17892.7	
testbench.sv	time	26340	cycle	2633	arg	a:183.035	b:14652.7	c:23991.4	res:8.84292e+21

Getting Started

- Break the problem down as much as you can
- You can ask ChatGPT how to implement commonly seen modules (ie. FIFO)
- Treat it as co-pilot: double check the generated code to verify that it makes sense


Solution

Approaching the Challenge

1. Submodule latencies
2. Calculate the formula
3. Add flow control

Finding the Latencies of Submodules

- Use what's provided!

 

tesbench.sv

```
module testbench;

//-----
// Signals to drive Device Under Test - DUT

logic          clk;
logic          rst;

logic          arg_vld;
wire           arg_rdy;

logic [FLEN - 1:0] a;
logic [FLEN - 1:0] b;
logic [FLEN - 1:0] c;

wire           res_vld;
logic          res_rdy;

wire [FLEN - 1:0] res;

//-----

// If we change FLEN to 32, we have to change these constants

localparam [FLEN - 1:0] inf      = 64'h7FF0_0000_0000_0000,
                      neg_inf    = 64'hFFF0_0000_0000_0000,
                      zero       = 64'h0000_0000_0000_0000,
                      nan        = 64'h7FF1_2345_6789_ABCD;

//-----

// Instantiating DUT

challenge dut (.*);
```

fpu_tb.sv

```
module fpu_tb (
);

reg          clk;
reg          rst;

reg          up_valid;
reg [FLEN - 1:0] a;
reg [FLEN - 1:0] b;

wire [FLEN - 1:0] res;
wire down_valid, busy, error;

//wire  arg_rdy = ~busy;
wire  arg_rdy = 1;

//-----

// If we change FLEN to 32, we have to change these constants

localparam [FLEN - 1:0] inf      = 64'h7FF0_0000_0000_0000,
                      neg_inf    = 64'hFFF0_0000_0000_0000,
                      zero       = 64'h0000_0000_0000_0000,
                      nan        = 64'h7FF1_2345_6789_ABCD;

//-----

// Instantiating DUT

f_mult dut (.*);
```

I/O are different!

```
//f_sub dut (.*);
```

```
//f_add dut (.*);
```

```
//-----
```

Output of simulation

```
***** Direct testing - a group of tests
fpu_tb.sv time    3700 cycle   369   arg a:0 b:0
fpu_tb.sv time    3710 cycle   370   arg a:1 b:10
fpu_tb.sv time    3720 cycle   371   arg a:4 b:40
fpu_tb.sv time    3730 cycle   372   arg a:13 b:130   res:0
fpu_tb.sv time    3740 cycle   373                                     res:10
fpu_tb.sv time    3750 cycle   374   arg a:40 b:400   res:160
fpu_tb.sv time    3760 cycle   375                                     res:1690
fpu_tb.sv time    3770 cycle   376                                     res:16000
fpu_tb.sv time    3780 cycle   377
```

3 cycles to produce output after the argument is accepted


f_mult - 3 cycle latency

f_sub - 3 cycle latency

f_add - 4 cycle latency


Designing a Suitable Architecture

$$a^{**5} + 0.3*b - c$$

 

Designing a Suitable Architecture

$$a^{**5} + 0.3*b - c$$

 

Adding Flow Control

